

## Model Question Paper-2 with effect from 2019-20 (CBCS Scheme)

USN

--	--	--	--	--	--	--	--	--	--

### Fourth Semester B.E. Degree Examination Subject Title: Analog Circuits

TIME: 03 Hours

Max. Marks: 100

Note: Answer any **FIVE** full questions, choosing at least **ONE** question from each **MODULE**.

Module -1			*Bloom's Taxonomy Level	Marks
Q.01	a	Derive the following relations with respect to small signal operation of BJT: i) Transconductance    ii) Voltage gain	L2	6
	b	A BJT having $\beta=100$ is biased at a DC collector current of 1mA. Find the value of $g_m$ , $r_e$ and $r_{\pi}$ at the bias point.	L3	6
	c	With the small signal equivalent model of MOSFET, derive an expression for voltage gain and transconductance.	L2	8
OR				
Q.02	a	Derive the following relations with respect to small signal operation of BJT: i) Input resistance    ii) Emitter resistance Also derive the relation between emitter and base resistance.	L2	8
	b	A MOSFET is to operate at $I_D=0.1\text{mA}$ and is to have $g_m=1\text{mA/V}$ . If $k_n' = 50\mu\text{A/V}^2$ . Find the required W/L ratio and the overdrive voltage.	L3	6
	c	State the disadvantage of fixed $V_{GS}$ biasing technique and explain how stability of operating point is achieved in drain to gate feedback resistor biasing technique in a MOSFET amplifier	L1, L2	6
Module-2				
Q.03	a	With a neat circuit diagram and ac equivalent circuit, derive the expressions for $R_{in}$ , $A_{v_o}$ , $A_v$ and $R_o$ for a Source follower.	L2	8
	b	A CS amplifier utilizes a MOSFET biased at $I_D=0.25\text{mA}$ with $V_{OV}=0.25\text{V}$ and $R_D=20\text{k}\Omega$ . The device has $V_A=50\text{V}$ . The amplifier is fed with a source having $R_{sig}=100\text{k}\Omega$ , and a $20\text{-k}\Omega$ load is connected to the output. Find $R_{in}$ , $A_{v_o}$ , $A_v$ and $R_o$ and $G_v$ . If to maintain reasonable linearity, the peak of the input sine-wave signal is limited to 10% of $(2V_{OV})$ what is the peak of the sinewave voltage at the output?	L3	8
	c	In an RC Phase shift oscillator, $R=200\text{k}\Omega$ and $C=200\text{pF}$ . Find the frequency of the BJT based oscillator.	L3	4
OR				
Q.04	a	Draw and explain the complete frequency response of a common source amplifier. Derive the expression for its lower cutoff frequency	L1,L2	10
	b	Find the midband gain $A_M$ , and the upper 3-dB frequency $f_H$ of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100\text{ k}\Omega$ . The amplifier has $R_G = 4.7\text{M}\Omega$ , $R_D = R_L = 15\text{ k}\Omega$ , $g_m=1\text{mA/V}$ , $r_o=150\text{k}\Omega$ , $C_{gs}=1\text{pF}$ and $C_{gd}=0.4\text{pF}$	L3	6
	c	Explain the working of a Colpitts oscillator.	L1	4
Module-3				

Q. 05	a	With a neat block diagram explain the working of a Voltage series feedback amplifier. How are the overall gain, input and output impedances affected in these amplifiers?	L1,L2	8
	b	Show how Gain can be desensitized and bandwidth increased with the application of negative feedback.	L3	8
	c	Draw the circuit of a practical Voltage Shunt (or transresistance) feedback amplifier and explain its working.	L2	4
OR				
Q. 06	a	Explain a Class B Output stage. Prove that the maximum conversion efficiency of a Class B transformer coupled amplifier is 78.5%.	L1,L2	8
	b	A transformer coupled class A power amplifier supplies to an $80\Omega$ load connected across the secondary of a step down transformer having a turns ratio 5:1. Determine the maximum power output for a zero signal collector current of 120mA.	L3	6
	c	What is cross over distortion? How can it be eliminated?	L2	6
<b>Module-4</b>				
Q. 07	a	Explain with a neat diagram and relevant expressions, an opamp voltage series feedback amplifier	L1,L2	8
	b	Explain the following: 1) Virtual ground 2) Opamp AC amplifier	L1	6
	c	For an opamp non-inverting amplifier using 741 IC with $R_L=1\text{ K}\Omega$ and $R_F=10\text{K}\Omega$ , $A=200,000$ ; $R_i=2\text{M}\Omega$ , $R_o=75\Omega$ , $f_o=5\text{ Hz}$ ; supply voltages $\pm 15\text{V}$ , output voltage swing = $\pm 13\text{V}$ , Compute $A_F$ , $R_{if}$ , $R_{of}$ , $f_F$ .	L3	6
OR				
Q. 08	a	Explain an Instrumentation amplifier using transducer bridge with relevant equations.	L1	8
	b	Explain the basic comparator circuit using an opamp. How can this circuit be used in an application as a zero crossing detector?	L1	6
	c	For a Schmitt trigger circuit; $R_1=150\Omega$ and $R_2=68\text{k}\Omega$ , $v_{in}=500\text{mVp-p}$ sine wave and saturation voltages are $\pm 14\text{ V}$ . Determine the threshold voltages $V_{ut}$ and $V_{it}$ . Draw the output waveforms.	L3	6
<b>Module-5</b>				
Q. 09	a	Explain the operation of 4-bit R-2R DAC with neat circuit. For the R-2R DAC, with $R=10\text{k}\Omega$ and $R_F=20\text{k}\Omega$ and $V_{REF}=5\text{V}$ , determine the output voltage when the inputs $b_0=b_1=5\text{V}$ and $b_2=b_3=0\text{V}$	L2,L3	8
	b	Explain the operation of a Successive -approximation ADC with neat circuit diagram.	L2	6
	c	Draw the circuit and frequency response of a first order low pass filter. Design a first order low pass filter to have a cutoff frequency of 1kHz with a passband gain of 2.	L1,L3	6
OR				
Q. 10	a	Draw and Explain the circuit and frequency response of a wide band-pass filter.	L1	6
	b	Explain the operation of a monostable multivibrator with relevant diagrams and waveforms.	L1,L2	8

	c	In the astable multivibrator $R_A=2.2k\Omega$ , $R_B=3.9k\Omega$ and $C=0.1\mu F$ . Determine the positive pulse width $t_c$ , negative pulse width $t_d$ and free-running frequency.	L3	6
--	---	---	----	---

\*Bloom's Taxonomy Level: Indicate as L1, L2, L3, L4, etc. It is also desirable to indicate the COs and POs to be attained by every bit of questions.